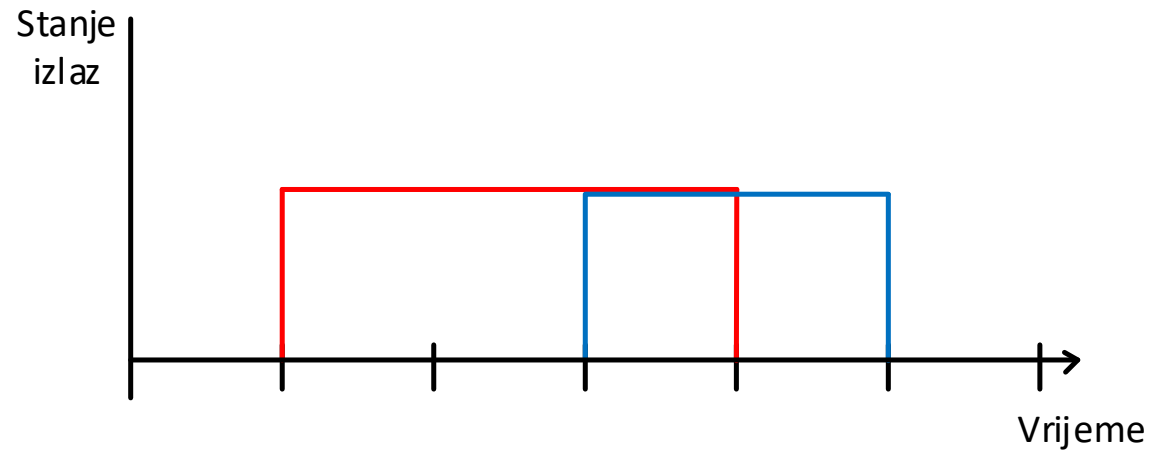


Arhitektura računalā


LV 8. Upravljanje portovima
I/O

Zadatak 1.

- Programiraj mikroupravljač da pali i gasi digitalne izlaze Arduina prema sljedećem grafu (pin 3 (crveni) i pin 8 (plavi))
- Jedan vremenski podiok iznosi 250 ms




ULAZ

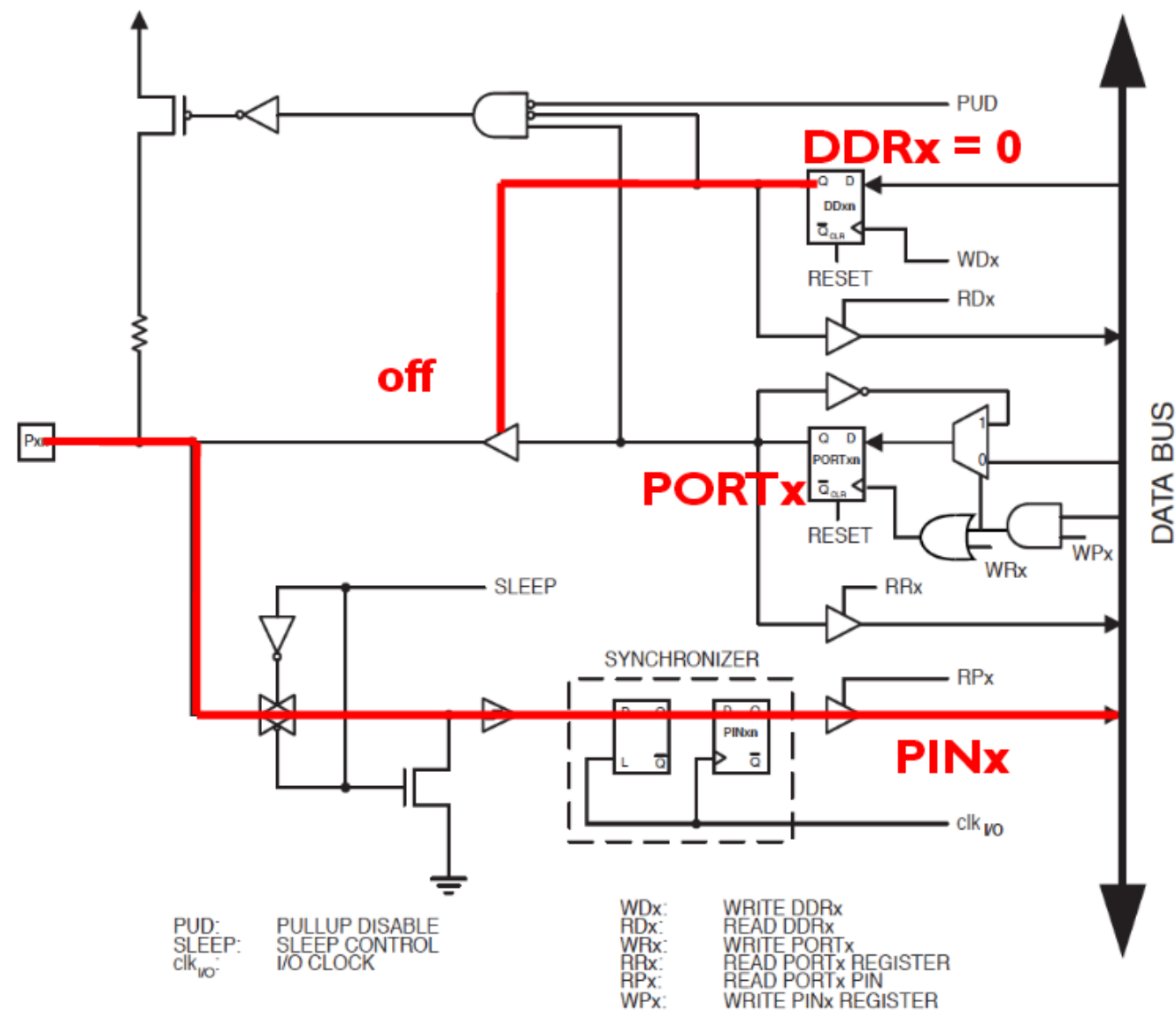

Naponska področja digitalnih ulaza

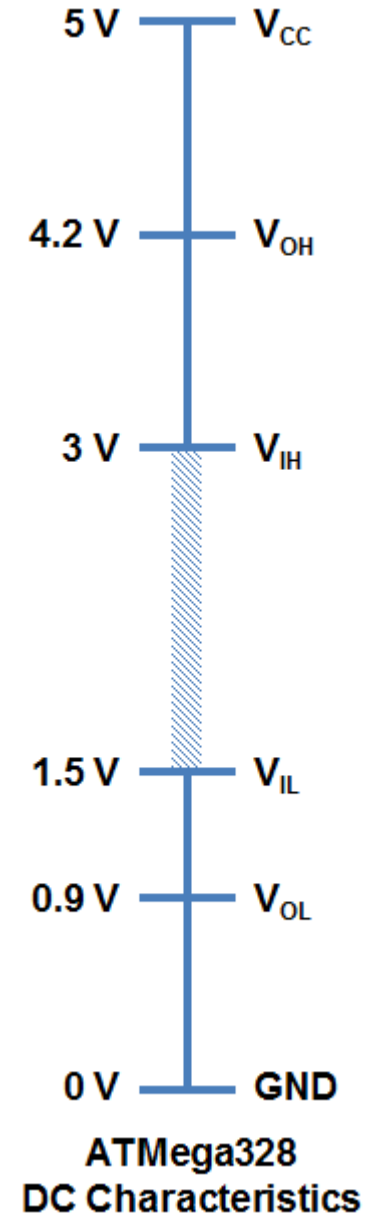- Logička jedinica "1"
 - 3V - 5V
- Logička nula "0"
 - 0 - 1.5V



Arduino Pin Mapping

www.arduino.cc

